

# FPGA Assignment 3

Guhan Rajasekar, Mtech ESE , 22410, DESE, IISc

## I INTRODUCTION

- This report is a summary on assignment 3 of the course *Digital System Design with FPGA*.

## II PIPELINED BOOTH MULTIPLIER

### 2.1 Pipelined Architecture

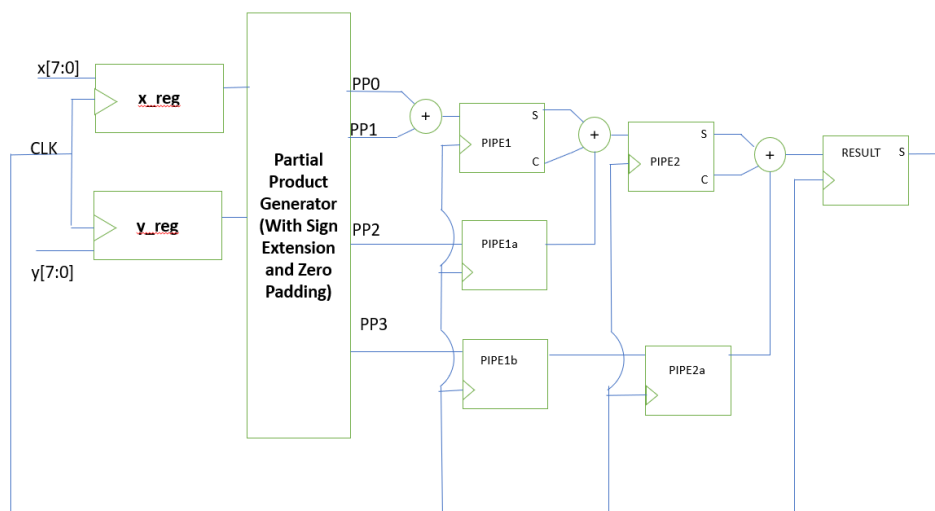


Figure 1: Block Diagram of Pipelined Booth Multiplier

- In the above block diagram, the reset signal has been omitted to keep the block diagram simple. However, all the clocked elements in the circuit also have a synchronous active low reset.

### 2.2 Post Route Timing Simulation Waveform

 


Figure 2: Post Route Timing Simulation of Pipelined Booth Multiplier

- The above waveform shows the simulation results that were obtained after implementation.

### 2.3 Resource Utilization of Un-pipelined Booth Multiplier

Name	^1	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (106)	BUFGCTRL (32)
N booth_multiplier		70	33	24	70	35	1

Figure 3: Resource Utilization Of Un-pipelined Booth Multiplier

### 2.4 Resource Utilization of Pipelined Booth Multiplier

Name	^1	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (106)	BUFGCTRL (32)
N booth_multiplier		67	64	29	67	35	1

Figure 4: Resource Utilization Of Pipelined Booth Multiplier

- The number of slice registers in the pipelined multiplier is more when compared with the number of slice registers in the un-pipelined booth multiplier.

### 2.5 RTL Schematic of the Pipelined Booth Multiplier

 


Figure 5: RTL Schematic of Pipelined Booth Multiplier

### 2.6 Delay Performance of Un-Pipelined Booth Multiplier

Design Timing Summary					
Setup		Hold		Pulse Width	
Worst Negative Slack (WNS): 0.048 ns		Worst Hold Slack (WHS): 0.070 ns		Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns		Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	
Total Number of Endpoints: 83		Total Number of Endpoints: 83		Total Number of Endpoints: 34	
All user specified timing constraints are met.					

Figure 6: Timing Summary of Un-pipelined Booth Multiplier

### 2.7 Delay Performance of Pipelined Booth Multiplier

Design Timing Summary					
Setup		Hold		Pulse Width	
Worst Negative Slack (WNS): 5.250 ns		Worst Hold Slack (WHS): 0.062 ns		Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns		Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	
Total Number of Endpoints: 188		Total Number of Endpoints: 188		Total Number of Endpoints: 95	
All user specified timing constraints are met.					

Figure 7: Timing Summary of pipelined Booth Multiplier

- Minimum possible  $T_{clk}$  of un-pipelined booth multiplier =  $10\text{ns} - 0.048\text{ns} = 9.952\text{ns}$ .
- Maximum operating frequency of un-pipelined booth multiplier =  $(1/9.952\text{ns}) = 100.482\text{MHz}$ .
- Minimum possible  $T_{clk}$  of pipelined booth multiplier is  $10\text{ns} - 5.25\text{ns} = 4.75\text{ns}$ .
- Maximum operating frequency of pipelined booth multiplier =  $(1/4.75\text{ns}) = 210.526\text{MHz}$ .
- As we can observe, the pipelined booth multiplier offers higher operating frequency than the un-pipelined booth multiplier.

### 2.8 Throughput of Pipelined Booth Multiplier

- Here, we define the throughput of the multiplier as the number of outputs that can be produced in unit time (1 second).
- At steady state, we can say that we get one output (one result) for every clock cycle.
- Hence we get one output for every  $4.75\text{ns}$ .
- So, the number of outputs obtained per unit time (in 1 second) is given by :

$$\frac{1}{4.75\text{ns}} = 210.526 * (10^6). \quad (1)$$

## III UP-DOWN COUNTER WITH SYNCHRONIZER AND DE-BOUNCER

### 3.1 Architecture of the Up-Down Counter

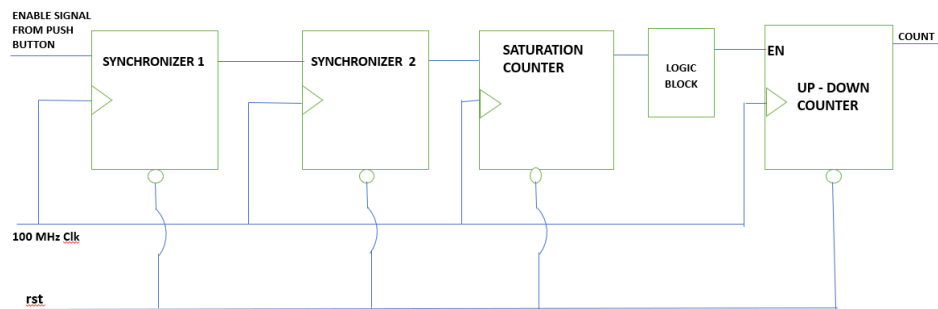


Figure 8: Architecture of Up-Down Counter

### 3.2 RTL Schematic

 


Figure 9: RTL Schematic of Up-Down Counter

- For clarity purposes, the RTL schematic is also submitted along with the report

### 3.3 Simulation Waveform of Up-Down Counter

 


Figure 10: simulation Waveform of Up-Down Counter

### 3.4 Timing Performance

Design Timing Summary			
Setup	Hold	Pulse Width	
Worst Negative Slack (WNS): 4.237 ns	Worst Hold Slack (WHS): 0.170 ns	Worst Pulse Width Slack (WPWS): 4.500 ns	
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns	
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	
Total Number of Endpoints: 59	Total Number of Endpoints: 59	Total Number of Endpoints: 29	
All user specified timing constraints are met.			

Figure 11: Timing Report of the Up-Down Counter

- Minimum  $T_{clk}$  is (10ns-4.237ns) = 5.763ns.
- As the slack is positive, we see that there are no timing violations

### 3.5 Resource Utilization of Up-Down Counter

Name	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (106)	BUFGCTRL (32)
modcounter	76	28	26	76	26	1

Figure 12: Resource Utilization of the Up-Down Counter

### 3.6 Design and Observations

- First the enable signal was given through one of the push buttons on the FPGA board.
- When this was done, it was observed that the count was incremented and decremented in a very erratic manner. This is due to mechanical de-bounce present in the switches of the FPGA board.
- First, to synchronize the asynchronous input, we used a two stage synchronizer.
- Then to overcome the de-bounce effect, the output of the synchronizer circuit was passed through a saturating counter.
- Whenever the button signal was read as high, this counter used to count up. And whenever the signal was low, the counter value was reset.
- At the end of 20ms, the status of enable signal was checked again. If it was high, it was considered as a valid press and appropriate action was taken.